
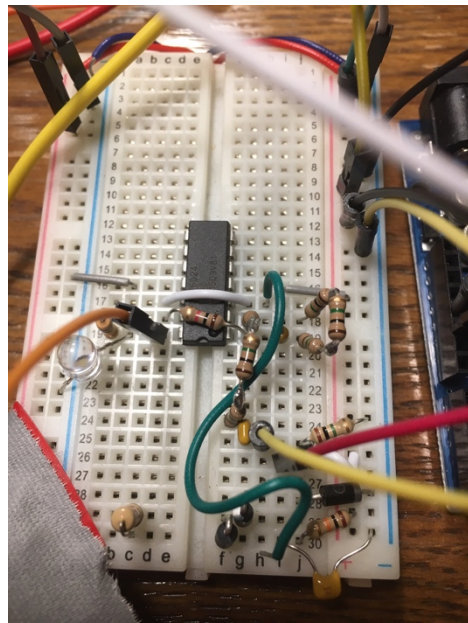


14-pin op-amp configuration


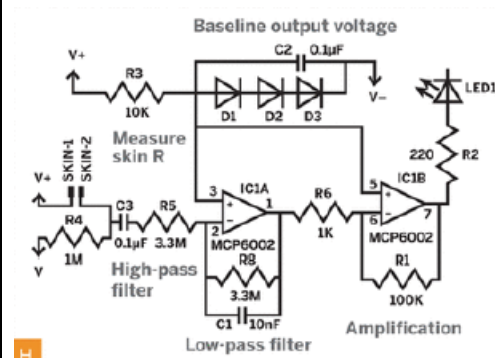


Truth Meter schematic



Close-up view of 14-pin op-amp breadboard configuration

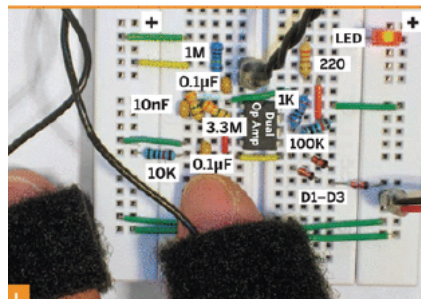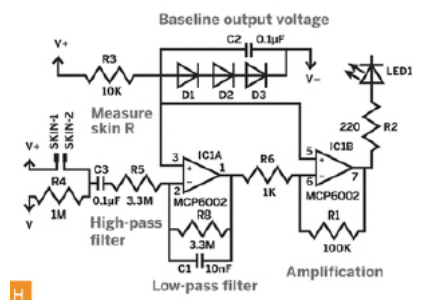Schematic of Truth Meter from MAKEVol26TruthMeter.pdf used for THEN GSR Game.



sourced from MAKEVol26TruthMeter.pdf